

LAB 2 – Mapping Your Circuit to an FPGA

Goals

- Design a 4-bit adder using structural modeling.
- Learn how to interface to the components on an FPGA Board.
- Implement your design on the Basys 3 FPGA board and see your circuit in action!

To Do

- The first step is designing a simple full adder, a 1-bit adder circuit.
- In the next step, you will instantiate 4 copies of the 1-bit adder to implement a “4-bit Adder”.
- Then, you will learn how to use Xilinx Vivado to write Verilog code and how to connect to the Basys 3 board.
- Finally, you will program the FPGA and get the circuit running on the FPGA board.
- Follow the instructions. Paragraphs that have a gray background like the current paragraph denote descriptions that require you to do something.
- **To complete the lab you have to show your work to an assistant before the deadline. There is nothing to hand in. The required tasks are clearly marked with gray background throughout this document.**

Introduction

In the previous lab we drew some small circuits. We did not, however, see what our circuit did. In today’s lab, we will see how we can implement our schematics on an FPGA board.

In the last week, our designs were relatively small. This week, we will design a slightly larger circuit using **structural modeling** (i.e., use explicit gate-level description), which we have already learned in class. First, we will design a small circuit that adds two 1-bit numbers. Then, we will combine multiple instances of the 1-bit adder circuit to make a larger 4-bit adder. This *hierarchical design technique* is very important to allow us to design more complex circuits.

Binary Addition

Today, we will start by designing a simple adder circuit. The following is a quick recap on a simple method to perform the addition of two binary numbers. Binary addition works in a very similar way to the decimal addition that you are used to. The only difference is that a digit in a binary number can only be 0 or 1, instead of an integer between 0 and 9.

Consider the following simple example:

$$\begin{array}{r}
 11 \\
 873 \\
 + 362 \\
 \hline
 1235
 \end{array}$$

1. We start from the right and first add $3 + 2$, which results in 5. Since this number is less than 10, we can directly write it as it is.
2. The next digit is $7 + 6$, which results in 13. Now we cannot directly write the result since it exceeds the largest possible number we can use in a digit. We write 3 to the result and have a 'carry' that we move over to the next digit.
3. In the third digit, we now have $1 + 8 + 3 = 12$ since we need to also add the carry from the right side. This result also produces a carry, which also gives the final result.

Now consider the very same addition when expressed with binary numbers.

$$\begin{array}{r}
 1 11 1 \\
 011 0110 1001 \\
 + 001 0110 1010 \\
 \hline
 100 1101 0011
 \end{array}$$

The principle is the same. We start from the right.

Add each digit:

1. $1 + 0$ is 1
2. $0 + 1$ is 1
3. $0 + 0$ is 0
4. ...

Once we try to add $1 + 1$ we realize that the result, $(2)_{10}$, cannot be expressed in one binary digit, $(10)_2$. This gives rise to a 'carry' signal that is propagated in the direction of the most significant bits.

Part 1 - One-bit addition

The example shows that adding two one-bit numbers requires two outputs: one ‘sum’ output that is the result of the addition, and a ‘carry-out’ output, that indicates that the addition overflowed and a carry signal was generated. This circuit is called a *half adder*.

The problem with the half adder is that it *produces* a ‘carry-out’ but *cannot accept* a ‘carry-in’ as an input. That is where the *full adder* circuit comes in. This is a circuit that can add three inputs (A, B, carry-in) and outputs the sum and carry-out signals.

By sequentially connecting the carry-out signal of one stage to the carry-in stage of the following digit we can build larger adders easily.

For your convenience, the questions from part 1 have been moved to a separate sheet at the end of this document.

Please answer those now.

Now we have everything in place to implement a 1-bit full adder in Vivado.

Part 2 - Starting Vivado and Creating a Project

Please follow the instructions below.

1. **Start Vivado:** Click on the Start menu and go to

Programs → Xilinx Design Tools → Vivado 2019.2.

Alternatively, searching for “Vivado 2019.2” using the search function in the task bar should also work.

2. **Create a ‘New Project’:** Inside Vivado, choose File → New Project. This will bring up a new project wizard.

- Specify the “Project name”. You can simply call it Lab2. You can also specify where the project files will be stored using the “Project location.” Click next.

- Select “RTL Project” as the project type and click next.

- In the “Add Source” dialog, just click next (we do not have source files yet).

- In the “Add Existing IP” dialog, click next.

- In the “Add Constraints” dialog, click next.

- In “Default Part”, we need to select the FPGA board that we are using. Type “xc7a35tcpg236-1” in the Search field and you should be left with only one option. Select it and click next.

- In “New Project Summary”, you can see the project configuration. Make sure that the default part and product family information reads:

Default Part: xc7a35tcpg236-1

Product: Artix-7


Family: Artix-7

Package: cpg236

Speed Grade: -1

Once everything checks out, click finish to create the project!

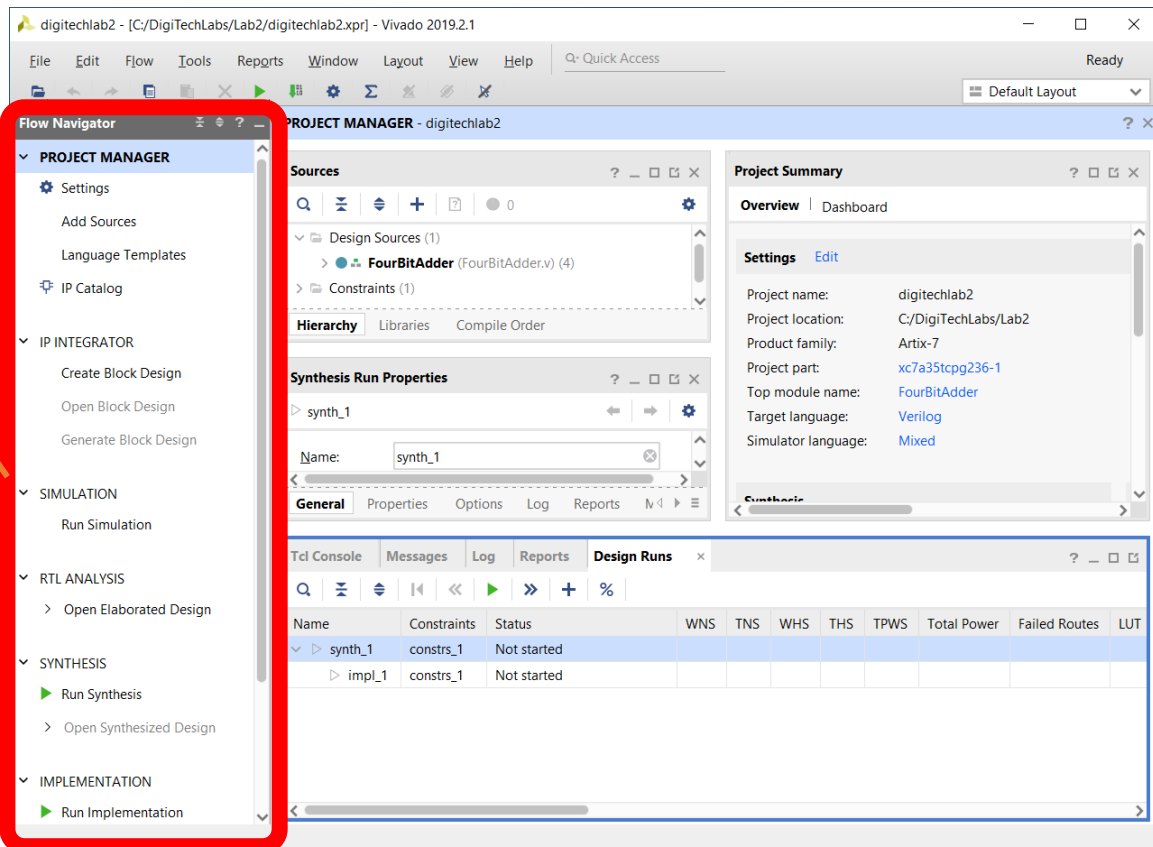After creating the project, you should see the following view:




On the left side of Vivado, you will find the “Flow Navigator”, which you will extensively use to develop your project and finally program it to the FPGA board.

Let’s create a new Verilog code file to implement the 1-bit full adder: inside the Flow Navigator, under “Project Manager”, click on “Add Sources”.

Select “Add or create design sources” and click next.

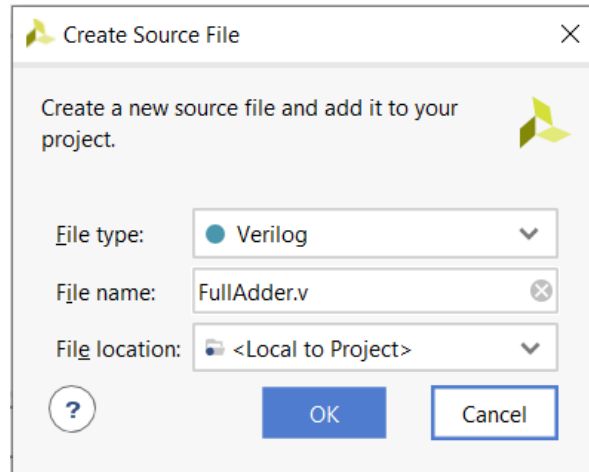Click “Create File”. A new dialog box will pop up:



Keep the type as Verilog and choose a file name for your 1-bit full adder – for example, “FullAdder.v”. Then click OK. The dialog will disappear, and you will see your design in the list. Click Finish. A new dialog will popup asking you to define the module. Simply skip this process and press OK and ignore the warning message.

In the Project Manager box, you should see your newly created file. Double click on it to edit it.

Now you can start implementing the Full Adder in Verilog!

Part 3 – Implementing a Full Adder in Verilog

First, we will need to specify the input and output of the full adder.

Complete the input/output list of the FullAdder module. Your code should look something like this:


```
module FullAdder(input a, input b, input ci, output s, output co);  
    <your logic here>  
endmodule
```

Implement the full adder logic inside the FullAdder module, using the equations you derived in Part 1. Notice that you MUST implement the FullAdder with logic gates (structural modeling). Otherwise (i.e., use behavior modeling by writing down the Boolean equation directly), points will be deducted.

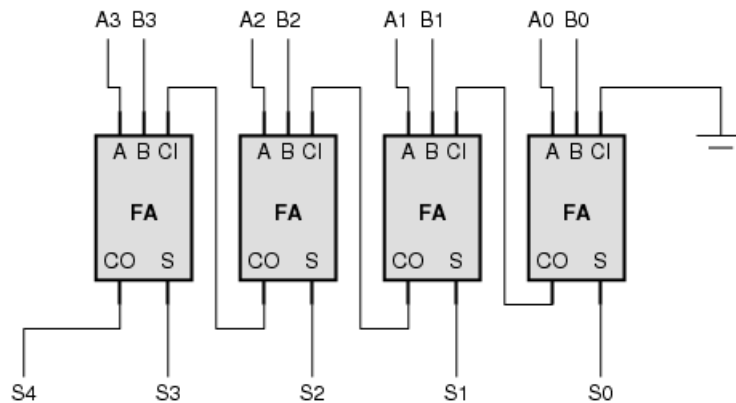Part 4 – Implementing a 4-Bit Adder in Verilog

Now that we have designed a full adder, we can use it to design a 4-bit adder.

We have two 4-bit numbers (A and B) in our adder. The output is the sum (S) of these two 4-bit numbers and is 5 bits wide, 4 Sum bits of the individual full adders plus the Carry Out bit of the final (left most, most significant) full adder. All but the first (right most, least significant) full adders have their Carry In signals connected to the Carry Out of the full adder to their left. The first (right most, least significant) full adder does not have anything to its right, so there is no Carry In entering this full adder. We can connect the Carry In input to logic-0. You can see an example in the following figure.



In the description (and the figure) the organization is so that the least significant bit is on the right and the most significant bit is on the left. This is partly for didactic purposes; the organization mimics the way we write numbers on paper.

Given the description, we can now start a Verilog code that contains four instances of the full adder (FA).

Similar as before, create another source file. You can call it FourBitAdder.v. Again, you should first complete the input/output list so that your code looks like:


```
module FourBitAdder(input [3:0] a, input [3:0] b, output [4:0] s);  
    <your logic here>  
endmodule
```

Afterwards, implement the combinational logic of the 4-bit adder by creating 4 instances of the full adder.

 Part 5 – Running Your 4-Bit Adder on the Basys 3 FPGA Board

After designing the 4-bit adder, we can now program it to the FPGA board. An FPGA is a reconfigurable chip that allows you to map a given schematic (essentially a netlist of interconnected logic gates) in itself. Different FPGAs can map anywhere from a few hundred to up to more than a million gates.

In this course, we will be using the Basys 3 boards from Digilent, shown below:



This board includes an Artix®-7 FPGA chip which we can program, some switches, some light-emitting diodes (LEDs), and some other cool features. You can learn more about the Basys 3 Starter Board from:

<http://store.digilentinc.com/basys-3-artix-7-fpga-trainer-board-recommended-for-introductory-users/>

In this lab we have two four-bit inputs that we can map to eight switches (e.g., labeled SW7 to SW0), and a 5-bit output which we can map to the LEDs (e.g., LD4 to LD0). From the board's reference manual,

https://reference.digilentinc.com/_media/basys3:basys3_rm.pdf

we find out to which FPGA pins the switches and the LEDs are connected (page 15). If you look at the board, you see that the pin numbers are also written next to the name of the LEDs and Switches. For example, the right most switch (SW0) is connected to pin V17.

What we now need to do is tell Vivado to which pin each of input and output should be connected. This is done using a Xilinx Design Constraint File (XDC). Typically, an XDC also contains timing related constraints, e.g., to indicate to Vivado how fast a circuit should run. For now, we do not need this functionality.

You can generate an XDC file the same way you generated a new source file, through *Add Sources* and then *Add or Create Constraints*, under *Project Manager*.

Once you have generated the new file, you will find it under “Constraints”, in the Project Manager.

If you double click on this entry you should start a text editor. Using the text editor, enter the following constraints:

```
set_property PACKAGE_PIN V17 [get_ports {a[0]}]
set_property PACKAGE_PIN V16 [get_ports {a[1]}]
set_property PACKAGE_PIN W16 [get_ports {a[2]}]
set_property PACKAGE_PIN W17 [get_ports {a[3]}]
set_property PACKAGE_PIN W15 [get_ports {b[0]}]
set_property PACKAGE_PIN V15 [get_ports {b[1]}]
set_property PACKAGE_PIN W14 [get_ports {b[2]}]
set_property PACKAGE_PIN W13 [get_ports {b[3]}]
set_property PACKAGE_PIN U16 [get_ports {s[0]}]
set_property PACKAGE_PIN E19 [get_ports {s[1]}]
set_property PACKAGE_PIN U19 [get_ports {s[2]}]
set_property PACKAGE_PIN V19 [get_ports {s[3]}]
set_property PACKAGE_PIN W18 [get_ports {s[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {a b s}]
```

Each line of code connects one of your inputs or outputs to a corresponding pin, which in turn connects your circuit to the peripherals on the board once it is downloaded to the FPGA. The last line sets the I/O standard of the ports. In this lab we will not get into the nitty-gritty of this, so simply include all the variable names in the last line.

Programming the FPGA. We are almost done —we now have to compile (map) our design onto the FPGA. This process consists of several independent steps (we do not discuss them in detail here), but you can use a shortcut:

Select your circuit (FourBitAdder) in *Project Manager*. From the *Flow Navigator*, select *Program and Debug → Generate Bitstream*.

This will generate a binary file, which is the FPGA programming file that you will later download to the FPGA. To generate the programming file, all other steps (i.e., Synthesis and Implementation) have to be completed.

You can track the process on the top right corner, where it will say “Running write_bitstream” with a progress bar. This process may take a couple of minutes. If there are errors or problems, try debugging your code or contact an assistant.

Now that we have the program file we need to transfer this information to the FPGA. Make sure the FPGA board is powered on and that it is connected to the computer through the USB cable.

From the *Flow Navigator*, select

Program and Debug → Open Hardware Manager → Open Target → Auto Connect

This will open a Hardware Manager.

Vivado should automatically detect the FPGA board. You are now ready to download the code to the board.

From the *Flow Navigator*, select

Program and Debug → Hardware Manager → Program Device → xc7a35t_0

A dialog window will pop up with two fields: Bitstream file and Debug probes file. The Bitstream file field should automatically contain the path of the previously generated bitstream file. Leave the Debug probes file empty. Press Program.

Now you are ready to test your circuit on the board. Use the switches and verify that your circuit functions correctly. Show the working circuit to an assistant. If there are errors, you should find the problem and correct it.

Last Words

We have (hopefully) managed to program the FPGA and have translated our design idea from paper, to Verilog code, to a physical working circuit.

It is quite possible that you have encountered errors during this exercise. The entire process consists of many steps, and at each step there are many parts where you could have made an error. If something did not work, starting at the lowest level, maybe...

- ...you made a mistake in the truth table?
- ...the equations were not derived correctly?
- ...there was a mistake in your Verilog implementation?
- ...there are errors in the constraint file?
- ...there are problems with the programming cable, or the USB port is not working?
- ...the configuration switches on the board were not correct?
- ...the board was not powered on?

Since many things can go wrong it is normal that you experience problems during this exercise. Don't feel frustrated: this is a complex process involving many steps, and getting it right requires some experience.

The circuit we created takes up a very small portion of the capabilities of the FPGA (it uses less than 1% of the FPGA's resources). For such a small circuit, some of the steps of the program may seem a little bit complex. However, the environment is designed for much larger circuits, and its quirks will start to make sense to you once you design more complex circuits.

Part 1a

The truth table below describes the operation of a full adder.

We use the inputs A, B, CI (carry-in) and the outputs are S (sum) and CO (carry-out).

Derive the Boolean equations for both outputs. Apply logic minimization techniques to come up with a simplified full adder circuit.

Then, **complete the truth table** by filling in the values of CO and S.

CI	B	A	CO	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\begin{aligned} CO &= AB\bar{CI} + A\bar{B}CI + \bar{A}BCI + ABCI \\ &= AB + CI(A\bar{B} + \bar{A}B) \\ &= AB + CI \cdot (A \oplus B) \end{aligned}$$

$$S = A \oplus B \oplus CI$$

Part 1b


Derive Boolean equations for CO and S (using whatever method you like).

$$CO = AB + CI \cdot (A \oplus B)$$

$$S = A \oplus B \oplus CI$$

Part 1c

 Draw the schematic of the full adder circuit according to the equations you have derived.



Appendix – Testing Your Circuit

You can verify the correctness of the circuit you implement in two ways: 1) program the FPGA with your circuit and just test it “in the field”, or 2) write a testbench to simulate your circuit in Vivado. We will introduce you to writing testbenches in Lab 6. However, if you want to try writing simple testbenches for your full adder (s), you can check the following tutorial: <https://fpgatutorial.com/how-to-write-a-basic-verilog-testbench/>